

PIDAC Antwoordblad - week 1

Naam: _____

1.2 Waarheidstabel

x	y	z	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

1.3 Wat gebeurt er als een ingang nergens op is aangesloten?

1.4 Schema

1.5 Waarheidstabel

Met welke poort komt dit overeen?

y	z	Q
0	0	
0	1	
1	0	
1	1	

1.6 Schema

Waarheidstabel

x	y	z	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

1.7 Waarheidstabel

Vereenvoudigd schema

x	y	Q
0	0	
0	1	
1	0	
1	1	

1.8 Schema

Waarheidstabel

y	z	Q
0	0	
0	1	
1	0	
1	1	

.

1.9 Schema

Waarheidstabel

x	y	z	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

.

1.10 Schema

Waarheidstabel

y	z	Q
0	0	
0	1	
1	0	
1	1	

.

1.11 Waarheidstabel

v	w	p	$\overline{v \cdot \overline{w}} \oplus p$	Q
0	0	0	$\overline{0 \cdot \overline{0}} \oplus 0 = \overline{0 \cdot 1} \oplus 0 = \overline{0} \oplus 0 = 1 \oplus 0 = 1$	
0	0	1	$\overline{0 \cdot \overline{0}} \oplus 1 = \overline{0 \cdot 1} \oplus 1 = \overline{0} \oplus 1 = 1 \oplus 1 = 0$	
0	1	0	$\overline{0 \cdot \overline{1}} \oplus 0 =$	
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Schema

1.12 Waarheidstabel

<i>a</i>	<i>b</i>	<i>c</i>	$\overline{\overline{a} + \overline{b}} + c =$	<i>Q</i>
0	0	0	$\overline{\overline{0} + \overline{0}} + 0 =$	
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

1.13 Schema

1.14 Schema